


# Ag Power and Equipment Technician

Electrical/Electronic Class  
Meters – Lab 3

Name \_\_\_\_\_  
Date \_\_\_\_\_

**Competency:** Understanding digital voltmeter (DVM) operation – amperage scale.

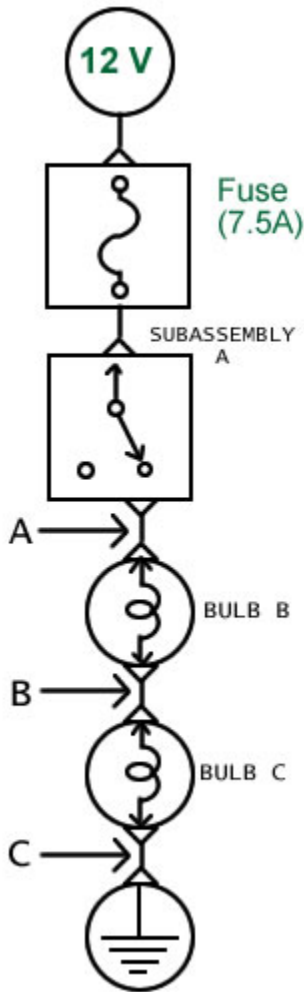**Directions:** Build the circuit shown below. Measure the current at each location in the circuit.



Current at A: \_\_\_\_\_

Current at B: \_\_\_\_\_

Current at C: \_\_\_\_\_

Instructor's Initials